



APPLICATION NOTE 130

Analog Switches Operate With 3V or 5V Supplies

Abstract: By adding a voltage doubler and voltage inverter, a single 3V or 5V power supply can produce the voltages necessary to improve the performance on a dual voltage analog switch. With the higher power supplies and wider range, the on resistance and timing performance are enhanced.

By adding a single component to a 3V-only or 5V-only board, you can operate conventional CMOS analog switches with performance approaching that specified with $\pm 15V$ supplies. This means fast switching, low on-resistance, CMOS/TTL compatibility, low power consumption, and a signal range ($\pm V_{CC}$) that exceeds the input supply range (V_{CC} to ground).

Simply add a charge-pump voltage converter (IC1), which produces $\pm 2V_{CC}$ outputs from a V_{CC} input. These unregulated voltages ensure reliable switch operation for V_{CC} levels as low as 3V. Logic thresholds for the switch remain unaffected.

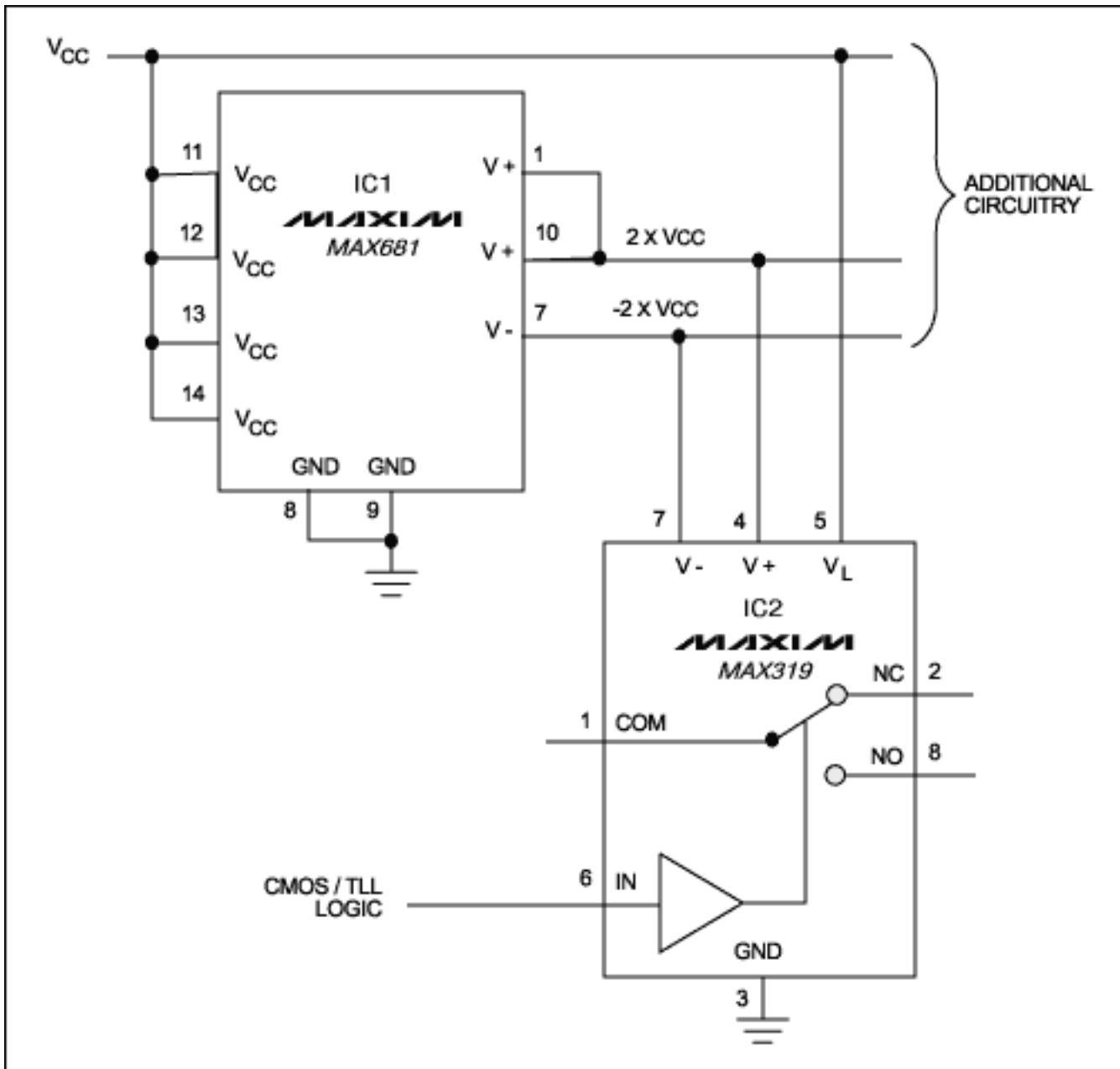


Figure 1. The charge pump (IC1) provides a local bipolar power supply for the CMOS analog switch (IC2).

A V_{CC} of 3V (for instance) produces $\pm 6V$ rails for the switch (IC2), resulting in on-resistance $< 30\Omega_W$, switching times $< 200ns$, leakage $< 0.1nA$, and I_{CC} current $< 0.5mA$. Raising V_{CC} to 5V produces $\pm 10V$ rails, resulting in on-resistance $< 20\Omega_W$, switching times $< 150ns$, leakage $< 0.4nA$, and I_{CC} current $< 1.3mA$.

IC1 can easily power additional switches and/or low-power op amps, but more than a few milliamps of load current degrades performance by lowering the unregulated supply rails.

Application Note 130: <http://www.maxim-ic.com/an130>

More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

Related Parts

MAX319: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX681: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)

AN130, AN 130, APP130, Appnote130, Appnote 130

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>